

Problem 1 ) With dataflow Verilog, describe the Generate/Propagate Unit, the Carry-Lookahead Unit, and the Summation Unit in Figure 1 as separate modules. Do not include delays in your models. We will add them later in the lab experiments. Use the module interfaces below as a guide. Gate-level schematics can be hard to read so you may find expressions (3) through (11) easier to follow.

\*\*\*This Generate-Propagate Unit for 4-bit carry-lookahead adder  
\* Computes the generate (G) and propagate (P) signals for each bit.  
\*/

```
module generate_propagate_unit (G, P, X, Y);  
output wire [3:0] G, P; // 4-bit Generate and Propagate outputs  
input wire [3:0] X, Y; // 4-bit inputs (X and Y)
```

```
// Compute Generate and Propagate signals for each bit  
assign G = X & Y; // Generate:  $g_i = x_i * y_i$   
assign P = X ^ Y; // Propagate:  $p_i = x_i \text{ XOR } y_i$   
endmodule
```

```
//////////
```

\* Carry Lookahead Unit for 4-bit carry-lookahead adder  
\* Computes the carry signals for each bit position based on G, P, and input carry.  
//////////

```
module carry_lookahead_unit (C, G, P, C0);  
output wire [4:1] C; // Carry outputs (C1, C2, C3, C4)  
input wire [3:0] G, P; // 4-bit Generate and Propagate inputs  
input wire C0; // Initial carry input (usually 0 or previous carry)
```

```
// This Compute carry signals for each bit position
```

```
assign C[1] = G[0] | (P[0] & C0);  
assign C[2] = G[1] | (P[1] & G[0]) | (P[1] & P[0] & C0);  
assign C[3] = G[2] | (P[2] & G[1]) | (P[2] & P[1] & G[0]) | (P[2] & P[1] & P[0] & C0);  
assign C[4] = G[3] | (P[3] & G[2]) | (P[3] & P[2] & G[1]) | (P[3] & P[2] & P[1] & G[0]) | (P[3] & P[2] & P[1] & P[0] & C0);  
  
endmodule
```

```

/* * Summation Unit for 4-bit carry-lookahead adder
* Computes the sum bits based on propagate signals and carry bits.
*/

```

```

module summation_unit (S, P, C);
output wire [3:0] S; // 4-bit Sum output
input wire [3:0] P, C; // 4-bit Propagate and Carry inputs

assign S = P ^ C // Shifted carry inputs to match each bit position

endmodule

```

Question 2 ) Now, use structural Verilog along with the modules you have just created to wire up a 4-bit Carry Lookahead adder. The module interface you should use is provided below.

```

// Top-level module for a 4-bit Carry-Lookahead Adder (CLA)
module carry_lookahead_4bit(Cout, S, X, Y, Cin);

// Output ports
output wire Cout; // Carry-out of the 4-bit adder
output wire [3:0] S; // 4-bit sum output

// Input ports
input wire [3:0] X, Y; // 4-bit input operands
input wire Cin; // Input carry

// Internal wires for generate and propagate signals
wire [3:0] G, P; // Generate (G) and Propagate (P) signals for each bit
wire [4:1] C; // Carry signals between each bit stage (C[4] is final carry)

// Module instantiations
generate_propagate_unit GPU (.G(G), .P(P), .X(X), .Y(Y)); // Generate and propagate signals
carry_lookahead_unit CLA (.C(C), .G(G), .P(P), .C0(Cin)); // Carry lookahead logic
summation_unit SU (.S(S), .P(P), .C(C[3:0])); // Summation logic for each bit

// Final carry-out assignment
assign Cout = C[4]; // Connect final carry to the output
endmodule

```

Question 3 ) What is the gate-count of your 4-bit carry-lookahead adder?

**The gate count is 26**

Question 4 ) The previous problems were concerned with a single-level 4-bit carry-lookahead adder. In one of the lab experiments, we will construct a 16-bit, 2-level carry-lookahead adder. The following questions will prepare you for this exercise. What is the propagation delay of the 16-bit, 2-level carry-lookahead adder in Figure 2? Likewise, what is the gate-count?

 


Figure 2: Two-Level Carry-Lookahead Adder

The propagation delay of the 16-bit, two-level carry-lookahead adder is 6 gate delays.

The total gate count is calculated as follows:

$$32+14\times 4+14\times 4+16=188 \text{ gates}$$